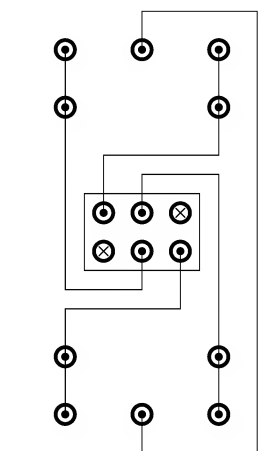


FROM POWER SUPPLY


RED (+) GRN BLK (-)



RED (+) GRN BLK (-)

TO MODULE

FROM POWER SUPPLY

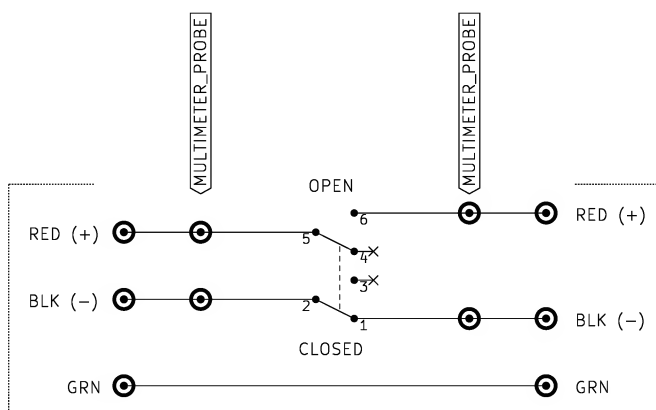

TO MODULE

*** Un!**

Title: Current Draw Box

This simple little box helps measure current draw on a module using a multimeter
The DPDT switch opens one rail for measurement while simultaneously closing the other
rail to power the module
Power connections are made using 4mm Banana Sockets for maximum compatibility

Size: A4

Date: 2017-08-28

Rev: V1

www.unrecordings.co.uk

Sheet: 1/1